

## Sallen and Key Filter

Sallen-Key Filter topology is used as the building block to implement higher order active filters

The **Sallen and Key Filter** design is a second-order active filter topology which we can use as the basic building blocks for implementing higher order filter circuits, such as low-pass (LPF), high-pass (HPF) and band-pass (BPF) filter circuits.

As we have seen in this filters section, electronic filters, either passive or active, are used in circuits where a signals amplitude is only required over a limited range of frequencies. The advantage of using *Sallen-Key Filter* designs is that they are simple to implement and understand.


The Sallen and Key topology is an active filter design based around a single non-inverting operational amplifier and two resistors, thus creating a voltage-controlled voltage-source (VCVS) design with filter characteristics of, high input impedance, low output impedance and good stability, and as such allows individual Sallen-key filter sections to be cascaded together to produce much higher order filters.

But before we look at the design and operation of the *Sallen-key filter*, let's first remind ourselves of the characteristics of a single resistor-capacitor, or RC network when subjected to a range of input frequencies.

### The Voltage Divider

When two (or more) resistors are connected together across a DC supply voltage, different voltage values will be developed across each resistor creating what is basically called a voltage divider or potential divider network.

### Resistive Voltage Divider

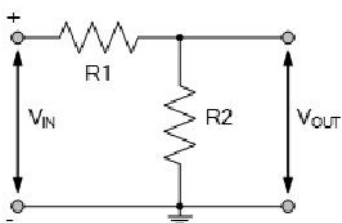

The basic circuit shown consists of two resistors in series connected across an input voltage,  $V_{IN}$ .

*Ohm's Law* tells us that the voltage dropped across a resistor is the sum of the current flowing through it multiplied by its resistive value,  $V = I \cdot R$ , so if the two resistors are equal, then the voltage dropped across both resistors,  $R1$  and  $R2$  will also be equal and is split equally between them.

The voltage developed or dropped across resistor  $R2$  represents the output voltage,  $V_{OUT}$  and is given by the ratio of the two resistors and the input voltage. Thus the transfer function for this simple voltage

divider network is given as:

## Resistive Voltage Divider Transfer Function

$$A_V = \frac{V_{OUT}}{V_{IN}} = \frac{R_2}{(R_1 + R_2)}$$


$$\text{Thus: } V_{OUT} = V_{IN} \frac{R_2}{(R_1 + R_2)}$$

But what would happen to the output voltage,  $V_{OUT}$  if we changed the input voltage to an AC supply or signal, and varied its frequency range. Well actually nothing, as resistors are generally not affected by changes in frequency (wirewounds excluded) so their frequency response is zero, allowing AC,  $I_{rms}^2 \cdot R$  voltages to be developed or dropped across the resistors just the same as it would be for steady state DC voltages.

## The RC Voltage Divider

If we change resistor  $R_1$  above to a capacitor,  $C$  as shown, how would that affect our previous transfer function. We know from our tutorials about **Capacitors** that a capacitor behaves like an open circuit once charged when connected to a DC voltage supply.

### RC Voltage Divider

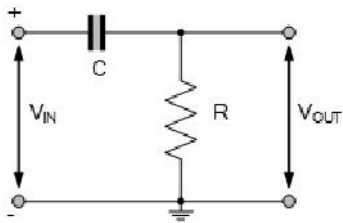

Thus when a steady state DC supply is connected to  $V_{IN}$ , the capacitor will be fully charged after 5 time constants ( $5T = 5RC$ ) and in which time it draws no current from the supply. Therefore there is no current flowing through the resistor,  $R$  and no voltage drop developed across it, so no output voltage. In other words, capacitors block steady state DC voltages once charged.

If we now change the input supply to an AC sinusoidal voltage, the characteristics of this simple RC circuit completely changes as the DC or constant part of the signal is blocked. So now we are analysing the RC circuit in the frequency domain, that is the part of the signal that depends on time.

In an AC circuit, a capacitor has the property of **capacitive reactance**,  $X_C$  but we can still analyse the RC circuit in the same way as we did with the resistor only circuits, the difference is that the impedance of the capacitor now depends on frequency.


For AC circuits and signals, capacitive reactance ( $X_C$ ), is the opposition to alternating current flow through a capacitor measured in Ohm's. Capacitive reactance is frequency dependant, that is at low frequencies ( $f \cong 0$ ) the capacitor behaves like an open circuit and blocks them

At very high frequencies ( $f \cong \infty$ ) the capacitor behaves like a short circuit and pass the signals directly to the output as  $V_{OUT} = V_{IN}$ . However, somewhere in between these two frequency extremes the capacitor has an impedance given by  $X_C$ . So our voltage divider transfer function from above becomes:

$$A_V = \frac{V_{OUT}}{V_{IN}} = \frac{R}{(R + X_C)}$$

Thus changes in frequency, causes changes in  $X_C$ , which causes changes in the magnitude of the output voltage. Consider the circuit below.

## RC Filter Circuit

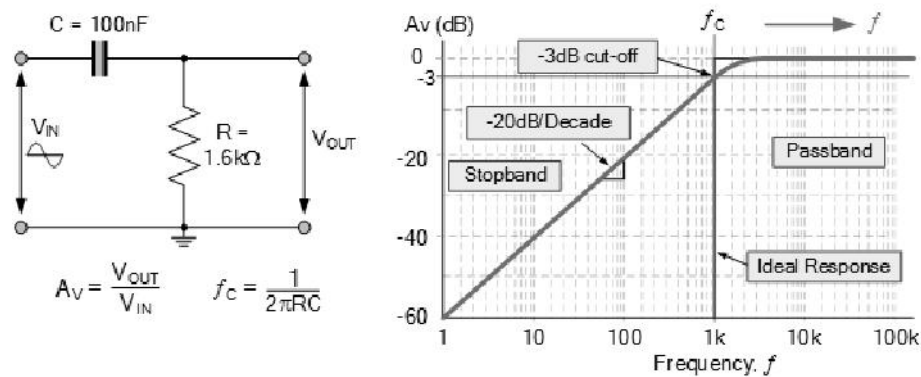

The graph shows the frequency response of this simple 1<sup>st</sup>-order RC circuit. At low frequencies the voltage gain is extremely low, as the input signal is being blocked by the reactance of the capacitor. At high frequencies the voltage gain is high (unity) as the reactance causes the capacitor to effectively become a short-circuit to these high frequencies, so  $V_{OUT} = V_{IN}$ .

However, there becomes a frequency point where the reactance of the capacitor is equal to the resistance of the resistor, that is:  $X_C = R$  and this is called the “critical frequency” point, or more commonly called the **cut-off frequency**, or **corner frequency**  $f_c$ .

As the cut-off frequency occurs when  $X_C = R$  the standard equation used to calculate this critical frequency point is given as:

### Cut-off Frequency Equation

$$f_c = \frac{1}{2\pi RC}$$

The cut-off frequency,  $f_c$  defines where the circuit, in this example, changes from attenuating or blocking all frequencies below,  $f_c$  and starts to pass all the frequencies above this  $f_c$  point. Thus the circuit is called a “high pass filter”.

The cut-off frequency is where the ratio of the input-to-output signal has a magnitude of 0.707 and when converted to decibels is equal to -3dB. This is often referred to as a filter's 3dB down point.

As the reactance of the capacitor is related to frequency, that is capacitive reactance ( $X_C$ ) varies inversely with applied frequency, we can modify the above voltage divider equation to obtain the transfer function of this simple RC high pass filter circuit as shown.

### RC Filter Circuit

$$\frac{V_{OUT}}{V_{IN}} = \frac{R}{(R + X_C)}$$

$$\text{As: } X_C = \frac{1}{2\pi f C}$$


$$\therefore \frac{V_{OUT}}{V_{IN}} = \frac{R}{\left(R + \frac{1}{2\pi f C}\right)} = \frac{2\pi f RC}{1 + 2\pi f RC}$$

One of the main disadvantages of an RC filter is that the output amplitude will always be less than the input so it can never be greater than unity. Also the external loading of the output by more RC stages or circuits will have an effect on the filter's characteristics. One way to overcome this problem is to convert the passive RC filter into an “Active RC Filter” by adding an operational amplifier to the basic RC configuration.

By adding an operational amplifier, the basic RC filter can be designed to provide a required amount of voltage gain at its output, thus changing the filter from an attenuator to an amplifier. Also due to the high input impedance and low output impedance of an operational amplifier prevents external loading of the filter allowing it to be easily adjusted over a wide frequency range without altering the designed frequency response.

Consider the simple active RC high-pass filter below.

## Active High Pass Filter

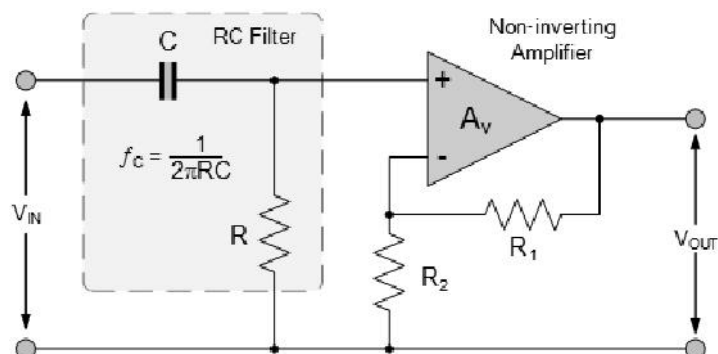

The RC filter part of the circuit responds the same as above, that is passing high frequencies but blocking low frequencies, with the cut-off frequency set by the values of R and C. The operational amplifier, or op-amp for short, is configured as a **non-inverting amplifier** whose voltage gain is set by the ratio of the two resistors,  $R_1$  and  $R_2$ .

Then the closed loop voltage gain,  $A_V$  in the passband of a *non-inverting operational amplifier* is given as:

## Cut-off Frequency Equation

$$A_V = 1 + \frac{R_1}{R_2}$$

## RC Filter Example No1

A simple 1<sup>st</sup>-order active high-pass filter is required to have a cut-off frequency of 500Hz and a passband gain of 9dB. Calculate the required components assuming a standard 741 operational amplifier is used.

From above we have seen that the cut-off frequency,  $f_C$  is determined by the values of R and C in the frequency-selective RC circuit. If we assume a value for R of 5k $\Omega$  (any reasonable value would do), then the value of C is calculated as:

$$f_C = \frac{1}{2\pi RC} = 500\text{Hz}$$

We choose  $R = 5\text{k}\Omega$

$$\therefore C = \frac{1}{2\pi f_C R} = \frac{1}{2\pi \times 500 \times 5000} = 63.65\text{nF}$$

The calculated value of C is 63.65nF, so the nearest preferred value used is 62nF.

The gain of the high pass filter in the passband region is to be +9dB which equates to a voltage gain,  $A_V$  of 2.83. Assume an arbitrary value for feedback resistor,  $R_1$  of 15k $\Omega$ , this gives a value for resistor  $R_2$  of:

$$9\text{dB} = 20\log(A)$$

$$\therefore A = 2.83$$


$$A = \frac{V_{\text{OUT}}}{V_{\text{IN}}} = 1 + \frac{R_1}{R_2} = 2.83$$

Assume a value of  $R_1 = 15\text{k}\Omega$

$$\therefore R_2 = \frac{R_1}{A-1} = \frac{15000}{2.83-1} = 8197\Omega$$

Again the calculated value of  $R_2$  is  $8197\Omega$ . The nearest preferred value would be  $8200\Omega$  or  $8.2\text{k}\Omega$ . This then gives us the final circuit for our active high-pass filter example of:

## High Pass Filter Circuit

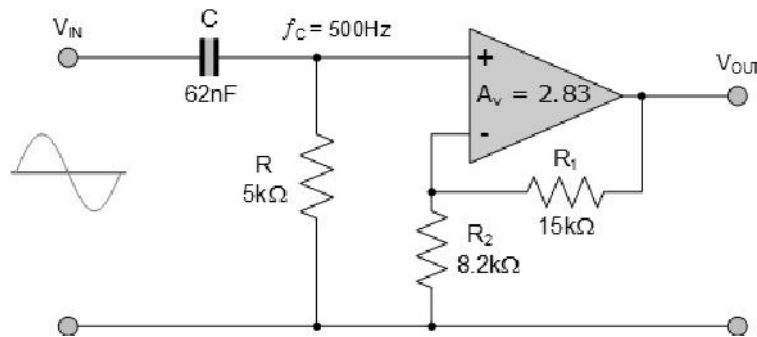


We have seen that a simple first-order high-pass filters can be made using a single resistor and capacitor producing a cut-off frequency,  $f_c$  point where the output amplitude is  $-3\text{dB}$  down from the input amplitude. By adding a second RC filter stage to the first, we can convert the circuit into a second-order high-pass filter.

## Second-order RC Filter

The simplest second order RC filter consists of two RC sections cascade together as shown. However, for this basic configuration to operate correctly, input and output impedances of the the two RC stages should not affect each others operation, that is they should be non-interacting.

## High Pass Filter Circuit

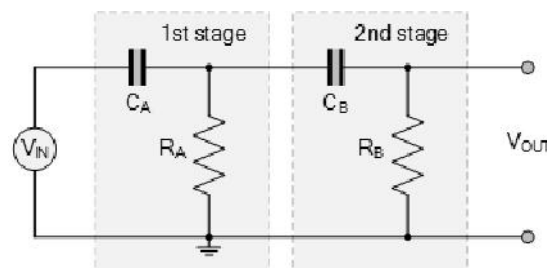

Cascading one RC filter stage with another (identical or different RC values), does not work very well because each successive stage loads the previous one and when more RC stages are added, the cut-off frequency point moves further away from the designed or required frequency.

One way to overcome this problem for a passive filter design is to have the input impedance of the second RC stage at least 10 times greater than the output impedance of the first RC stage. That is  $R_2 \geq 10 \cdot R_1$  and  $C_2 \geq 10 \cdot C_1$  at the cut-off frequency. More info

The advantage of increasing the component values by a factor of 10 is that the resulting second-order filter produces a steeper roll-off of 40dB/decade than cascaded RC stages. But what if you wanted to design a 4<sup>th</sup> or a 6<sup>th</sup>-order filter, then the calculation of ten times the value of the previous components can be time consuming and complicated.

One simple way to cascade together RC filter stages which do not interact or load each other to create higher-order filters (individual filter sections need not be identical) which can be easily tuned and designed to provide required voltage gain is to use *Sallen-key Filter* stages.

## Sallen and Key Filters

**Sallen-Key** is one of the most common filter configurations for designing first-order (1<sup>st</sup>-order) and second-order (2<sup>nd</sup>-order) filters and as such is used as the basic building blocks for creating much higher order filters.


The main advantages of the Sallen-key filter design are:

- Simplicity and Understanding of their Basic Design
- The use of a Non-inverting Amplifier to Increase Voltage Gain
- First and Second-order Filter Designs can be Easily Cascaded Together
- Low-pass and High-pass stages can be Cascaded Together
- Each RC stage can have a different Voltage Gain
- Replication of RC Components and Amplifiers
- Second-order Sallen-key Stages have Steep 40dB/decade roll-off than cascaded RC

However, there are some limitations to the basic Sallen-key filter design in that the voltage gain,  $A_V$  and magnification factor,  $Q$  are closely related due to the use of an operational amplifier within the Sallen-key design. Almost any  $Q$  value greater than 0.5 can be realised since using a non-inverting configuration, the voltage gain,  $A_V$  will always be greater than 1, (unity) but must be less than 3 otherwise it will become unstable.

The simplest form of Sallen-key filter design is to use equal capacitor and resistor values (but the C's and R's don't have to be equal), with the operational amplifier configured as a unity-gain buffer as shown. Note that capacitor  $R_A$  is no longer connected to ground but instead provides a positive feedback path to the amplifier.

## Sallen-key High Pass Filter Circuit

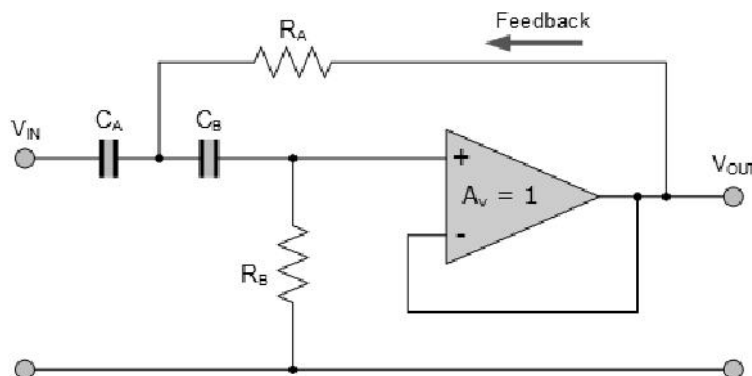

The passive components  $C_A$ ,  $R_A$ ,  $C_B$  and  $R_B$  form the second-order frequency-selective circuit. Thus at low frequencies, capacitors  $C_A$  and  $C_B$  appear as open circuits, so the input signal is blocked resulting in no output. At higher frequencies,  $C_A$  and  $C_B$  appear to the sinusoidal input signal as short circuits, so the signal is buffered directly to the output.

However, around the cut-off frequency point, the impedance of  $C_A$  and  $C_B$  will be the same value as  $R_A$  and  $R_B$ , as noted above, so the positive feedback produced through  $C_B$  provides voltage gain and an increase in output signal magnification,  $Q$ .

Since we now have two RC networks, the above equation for the cut-off frequency for a Sallen-Key filter is modified too:

## Sallen-key Cut-off Frequency Equation

$$f_c = \frac{1}{2\pi\sqrt{R_A R_B C_A C_B}}$$

If the two series capacitors  $C_A$  and  $C_B$  are made equal ( $C_A = C_B = C$ ) and the two resistors  $R_A$  and  $R_B$  are also made equal ( $R_A = R_B = R$ ), then the above equation simplifies to the original cut-off frequency equation of:

$$f_c = \frac{1}{2\pi RC}$$

As the operational amplifier is configured as a unity gain buffer, that is  $A = 1$ , the cut-off frequency,  $f_c$  and  $Q$  are completely independent of each other making for a simpler filter design. Then the magnification factor,  $Q$  is calculated as:


$$Q = \frac{1}{3 - A} = \frac{1}{3 - 1} = \frac{1}{2} = 0.5$$

Therefore for the unity-gain buffer configuration, the voltage gain ( $A_V$ ) of the filter circuit is equal to 0.5, or -6dB (over damped) at the cut-off frequency point, and we would expect to see this because its a second-order filter response, as  $0.7071 \times 0.7071 = 0.5$ . That is -3dB\*-3dB = -6dB.

However, as the value of  $Q$  determines the response characteristics of the filter, the proper selection of the operational amplifiers two feedback resistors,  $R_1$  and  $R_2$ , allows us to select the required passband gain  $A$  for the chosen magnification factor,  $Q$ .

Note that for a Sallen-key filter topology, selecting the value of  $A$  to be very close to the maximum value of 3, will result in high  $Q$  values. A high  $Q$  will make the filter design sensitive to tolerance variations in the values of feedback resistors  $R_1$  and  $R_2$ . For example, setting the voltage gain to 2.9 ( $A = 2.9$ ) will result in the value of  $Q$  being 10 ( $1/(3-2.9)$ ), thus the filter becomes extremely sensitive around  $f_c$ .

## Sallen-key Filter Response

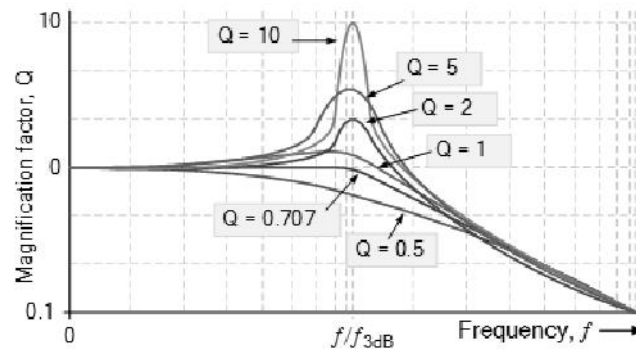

Then we can see that the lower the value of  $Q$  the more stable will be the Sallen and Key filter design. While high values of  $Q$  can make the design unstable, with very high gains producing a negative  $Q$  would lead to oscillations.

## Sallen and Key Filter Example No2

Design a second-order high-pass *Sallen and Key Filter* circuit with the following characteristics:  $f_c = 200\text{Hz}$ , and  $Q = 3$

To simplify the math's a little, we will assume that the two series capacitors  $C_A$  and  $C_B$  are equal ( $C_A = C_B = C$ ) and also the two resistors  $R_A$  and  $R_B$  are equal ( $R_A = R_B = R$ ).

$$f_c = \frac{1}{2\pi RC} = 200\text{Hz}$$

We will choose  $C = 100\text{nF}$

$$\therefore R = \frac{1}{2\pi f_c C} = \frac{1}{2\pi \times 200 \times 100 \times 10^{-9}} = 7957\Omega$$

The calculated value of  $R$  is  $7957\Omega$ , so the nearest preferred value used is  $8\text{k}\Omega$ .

For  $Q = 3$ , the gain is calculated as:

$$Q = \frac{1}{3 - A} \quad \therefore A = \frac{3Q - 1}{Q}$$

If  $Q = 3$ , then :

$$A = \frac{(3 \times 3) - 1}{3} = 2.667$$

If  $A = 2.667$ , then the ratio of  $R_1/R_2 = 1.667$  as shown.


$$A = \frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_1}{R_2} = 2.667$$

Assume a value of  $R_1 = 10\text{k}\Omega$

$$\therefore R_2 = \frac{R_1}{A - 1} = \frac{10000}{2.667 - 1} = 5998\Omega$$


The calculated value of  $R_2$  is  $5998\Omega$ , so the nearest preferred value used  $6000\Omega$  or  $6\text{k}\Omega$ . This then gives us the final circuit for our Sallen and Key high-pass filter example of:

## Sallen and Key High Pass Filter

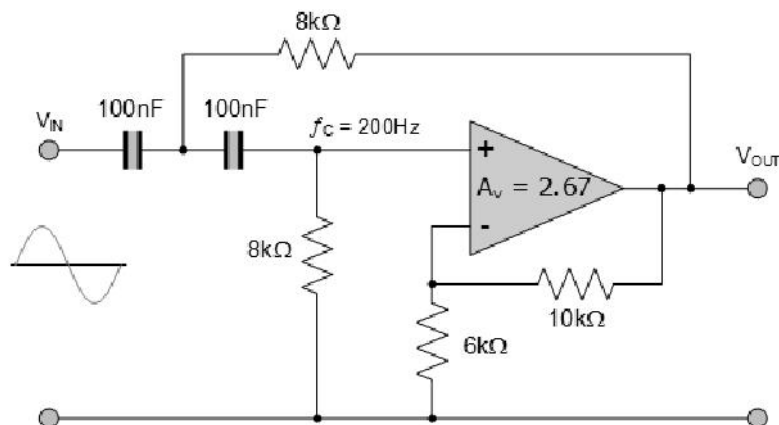

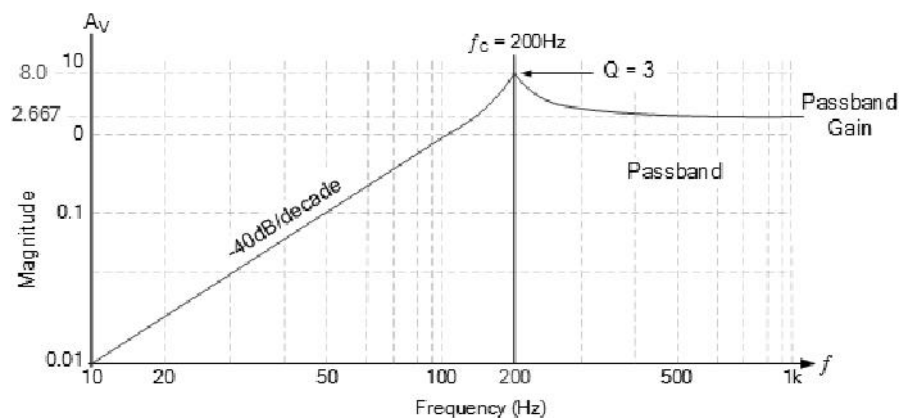Then with a cut-off or corner frequency of  $200\text{Hz}$ , a passband gain of  $2.667$ , and a maximum voltage gain at the cut-off frequency of  $8$  ( $2.667 \times 3$ ) due to  $Q = 3$ , we can show the characteristics of this second-order high-pass Sallen and Key filter in the following Bode plot.





## Sallen and Key Filter Summary

We have seen here in this tutorial that the Sallen-Key configuration, also known as a *voltage-controlled, voltage-source (VCVS)* circuit is the most widely used filter topologies due mainly to the fact that the operational amplifier used within its design can be configured as a unity gain buffer or as a non-inverting amplifier.

The basic Sallen-key filter configuration can be used to implement different filter responses such as, Butterworth, Chebyshev, or Bessel with the correct selection of RC filter network. Most practical values of R and C can be used remembering that for a specific cut-off frequency point, the values of R and R are inversely proportional. That is as the value of R is made smaller, C becomes larger, and vice versa.

The Sallen-key is a 2<sup>nd</sup>-order filter design which can be cascaded together with other RC stages to create higher-order filters. Multiple filter stages need not be the same but can each have different cut-off frequency or gain characteristics. For instance, putting together a low-pass stage and a high-pass stage to create a Sallen and Key band-pass filter.

Here we have looked at designing a Sallen-key high-pass filter, but the same rules apply equally for a low-pass design. The voltage gain,  $A_V$  of the op-amp determines its response and is set by the voltage divider resistors,  $R_1$  and  $R_2$  remembering that the voltage gain must be less than 3 otherwise, the filter circuit will become unstable.

## 3 Comments

Join the conversation

Your Name

Email Address

Write your comment here

☐ Notify me of follow-up comments by email.

SUBMIT



Joe

how is the equation for Q developed?  $Q = 1/(3-A)$  ie: where did the value (3) come from?

Posted on January 05th 2020 | 10:13 pm

← Reply



Wayne Storr

As explained in the tutorial, voltage gain,  $A_v$  must be greater than 1 and less than 3, otherwise it will become unstable.

Posted on January 06th 2020 | 10:05 pm

← Reply



Pooja

How do I cite this page? Is bibtex available for this?

Posted on November 13th 2019 | 2:53 am

← Reply